

Ioannis Tsagkatakis
Karim Sherif


Real Time Filter Implementation On FPGA board




Part 1 Hardware Design

- Filter bank
 - Filter Chooser
 - Multiplier
 - Adder
 - Zipper
- Cache mem
 - Fifo_buffer_3
 - FIFO IP Core
- Filter Controller
- Controller Enable


Top Level

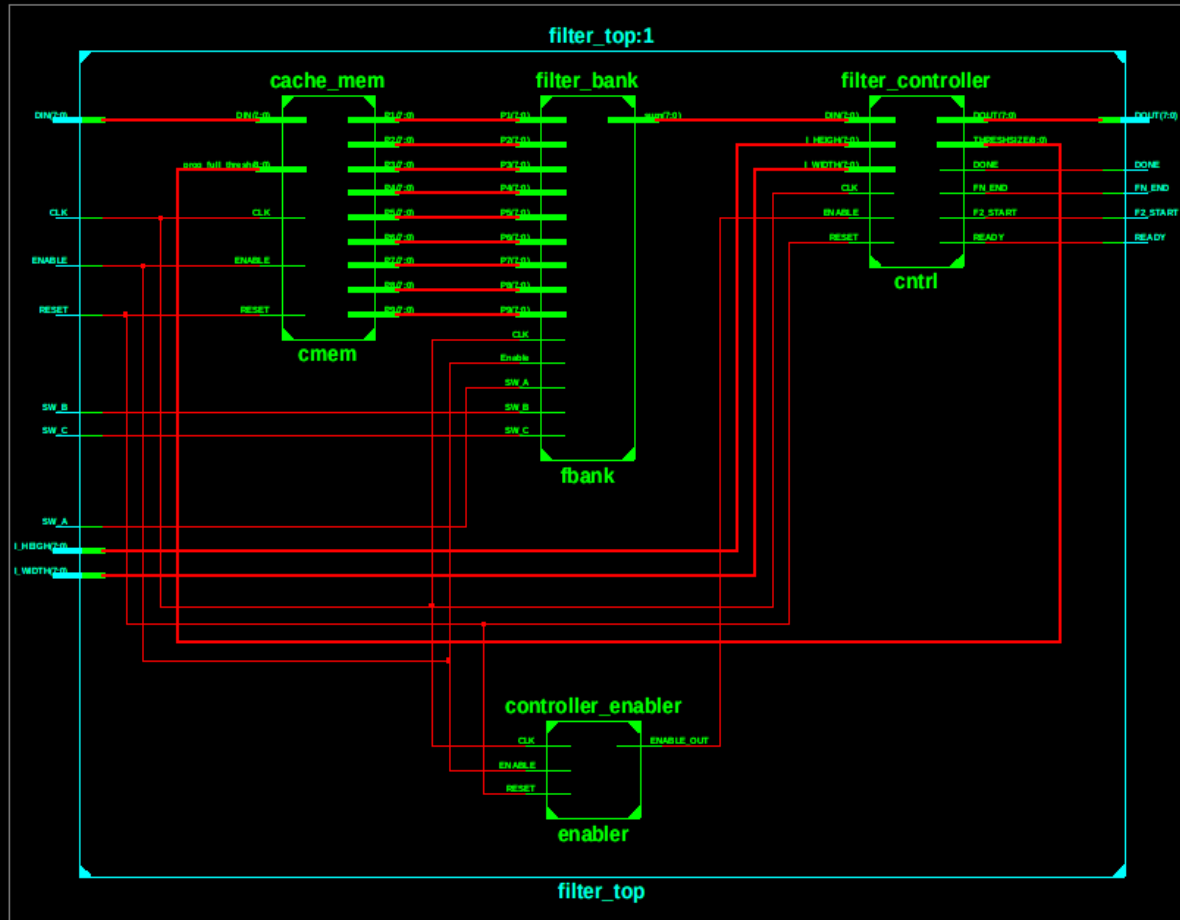



Top Level :: CacheMem

 


Top Level :: CacheMem :: Fifo Buffer

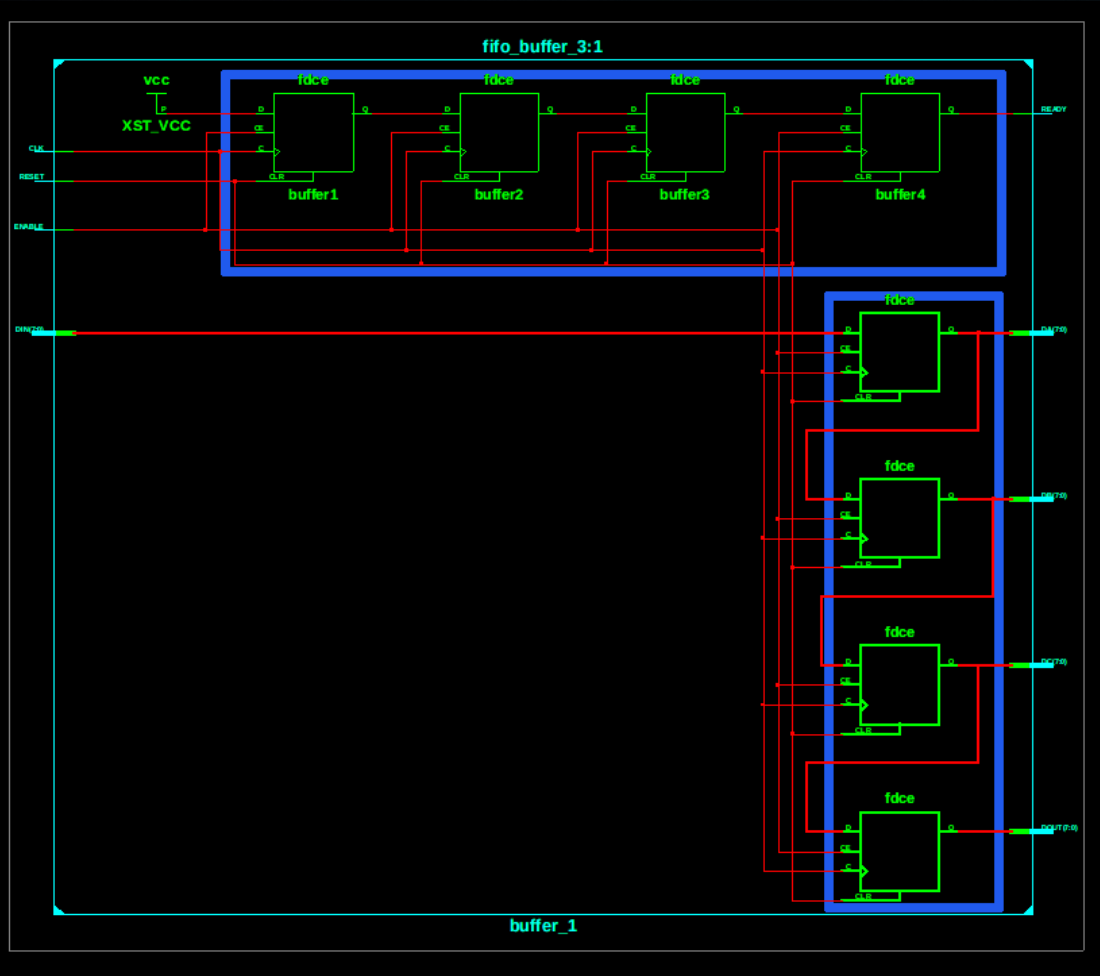


Top Level :: Filter Bank

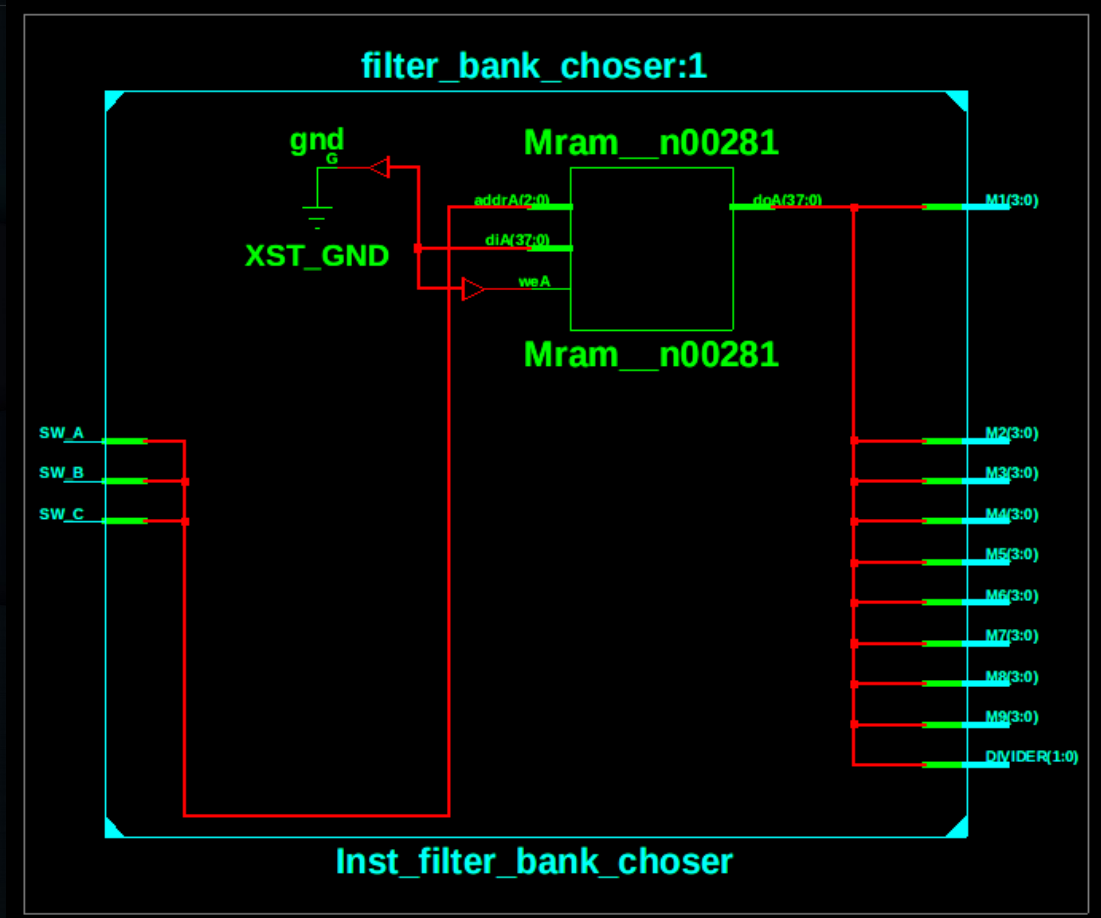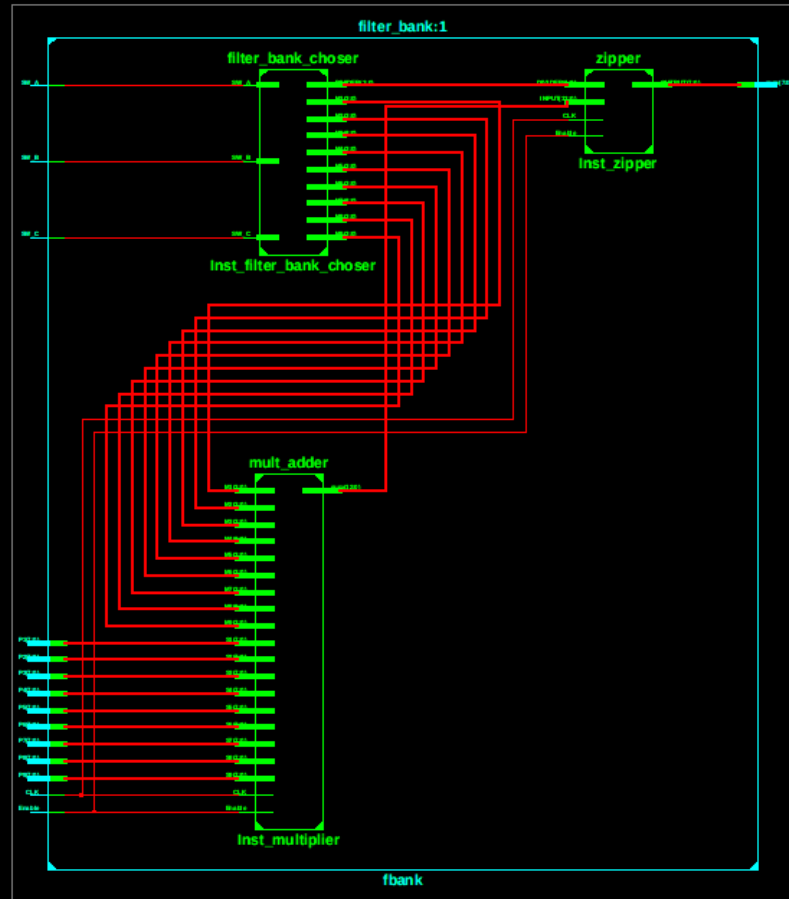


Top Level :: Filter Bank :: Zipper

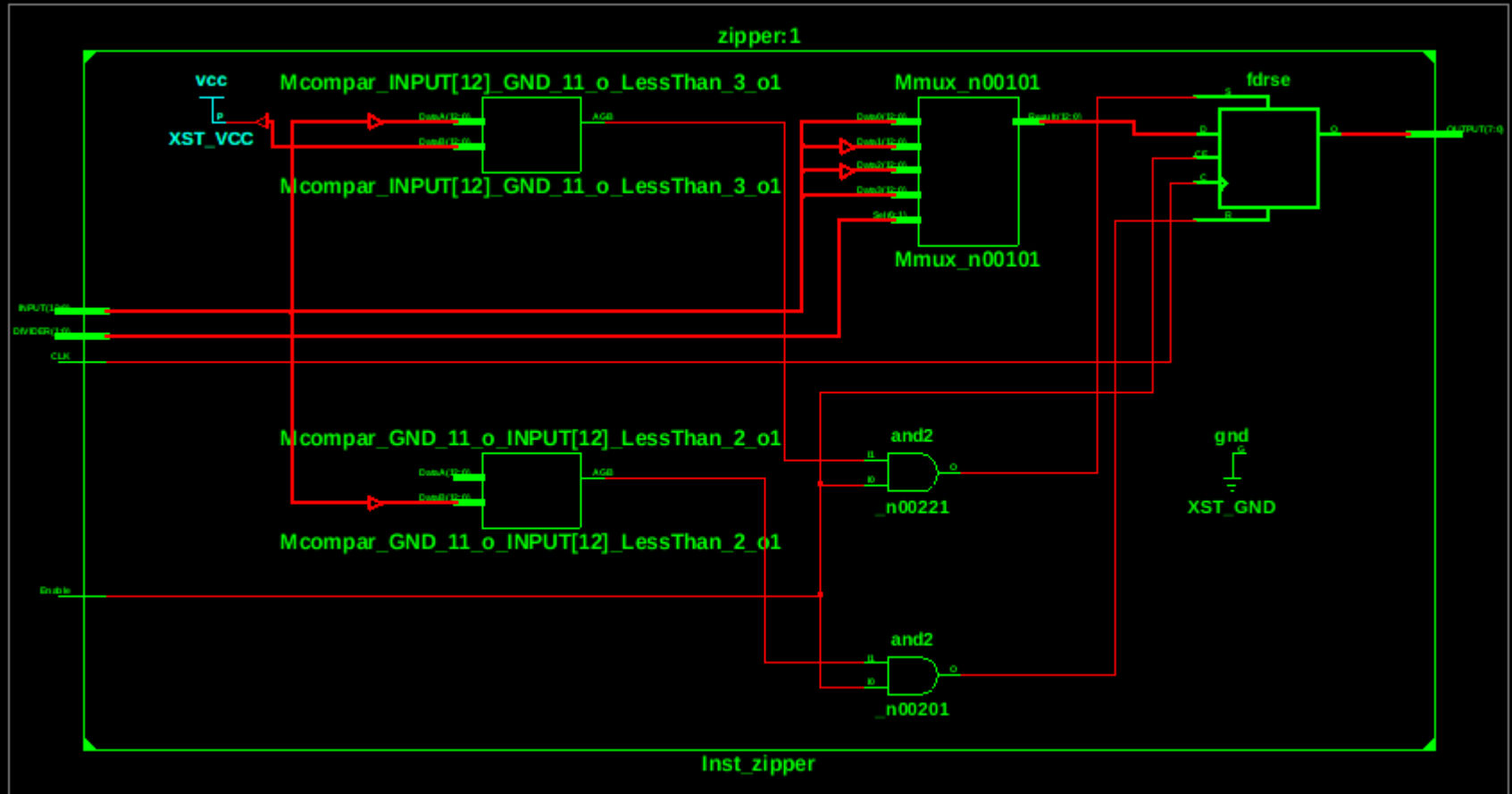


Top Level :: Filter Bank :: MADD

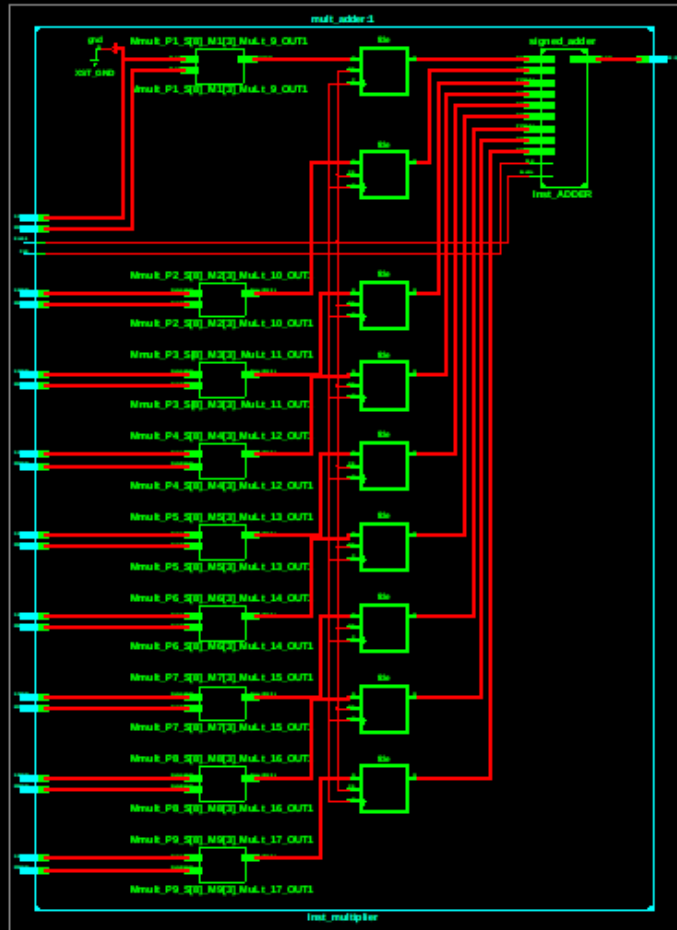

Top Level::Filter Bank :: MADD:: ADD

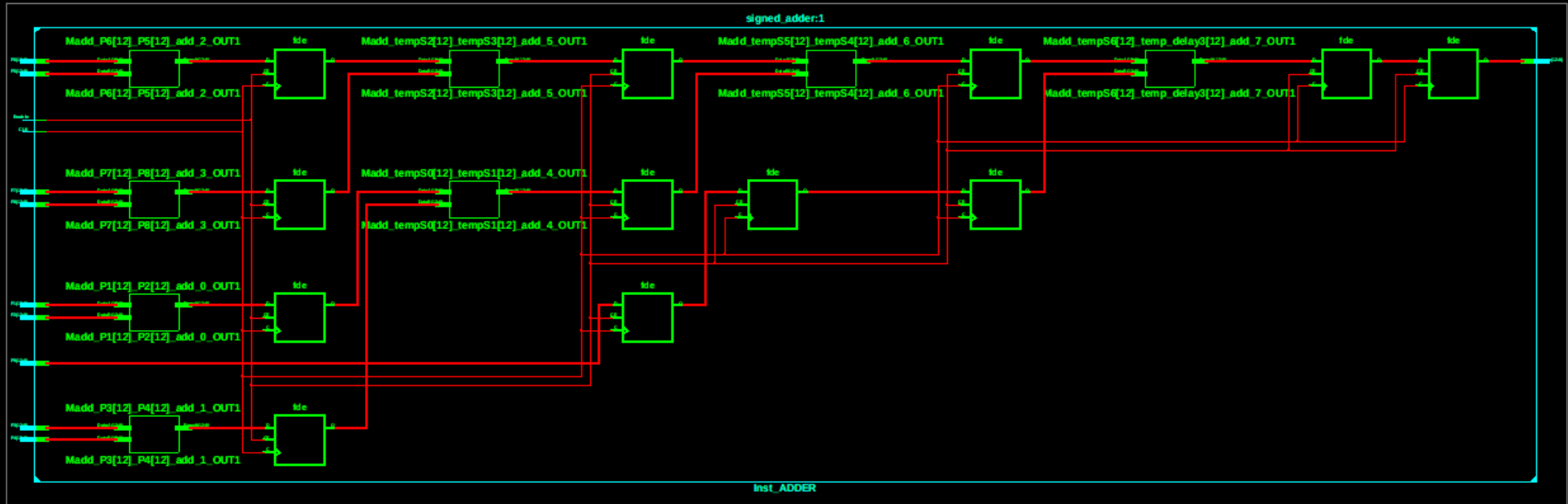

Top Level :: Control Logic

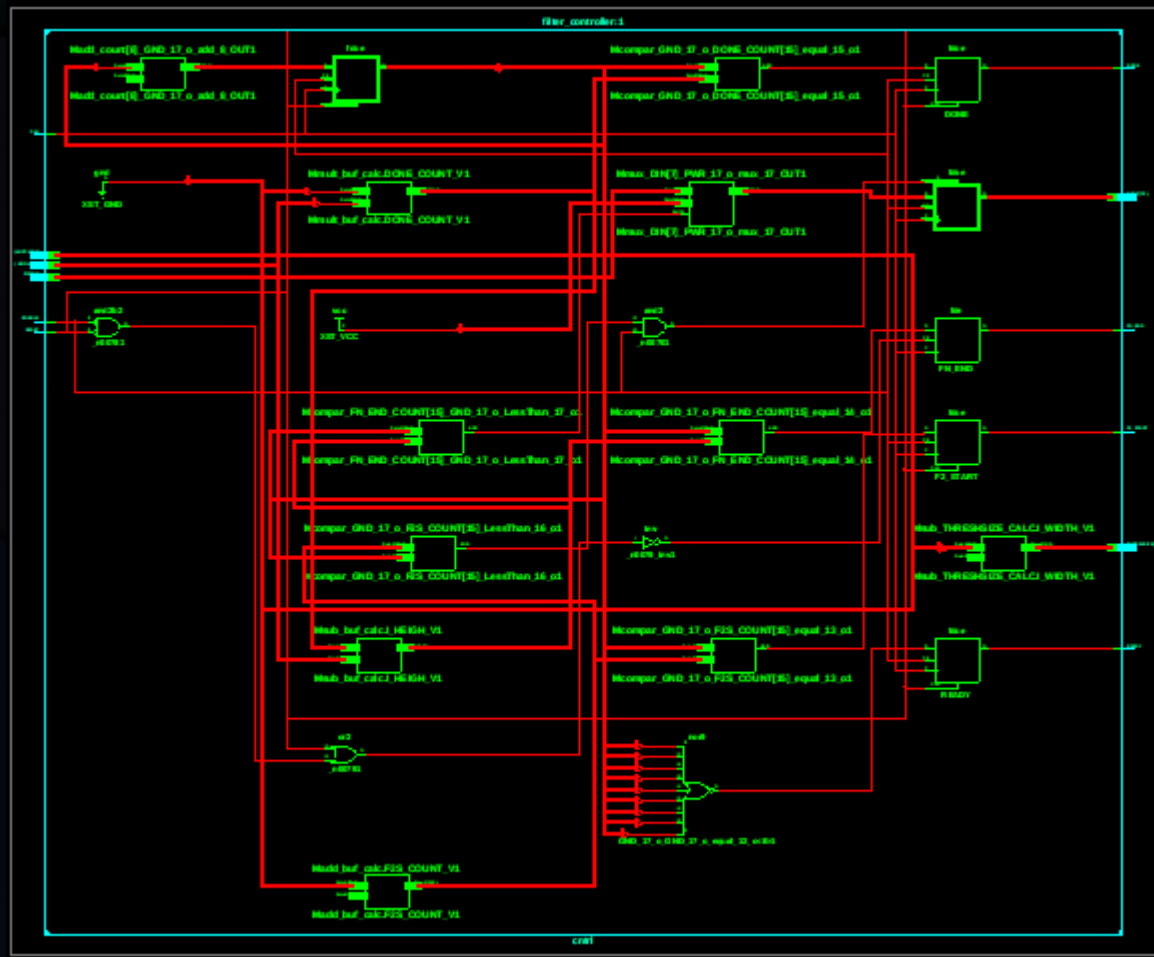

Top Level :: Control Logic

	1	2	3	4	5	6	7	8	9	10
1	0	1	2	3	4	5	6	7	8	9
2	10	11	12	13	14	15	16	17	18	19
3	20	21	22	23	24	25	26	27	28	29
4	30	31	32	33	34	35	36	37	38	39
5	40	41	42	43	44	45	46	47	48	49
6	50	51	52	53	54	55	56	57	58	59
7	60	61	62	63	64	65	66	67	68	69
8	70	71	72	73	74	75	76	77	78	79
9	80	81	82	83	84	85	86	87	88	89
10	90	91	92	93	94	95	96	97	98	99
11	100	101	102	103	104	105	106	107	108	109
12	110	111	112	113	114	115	116	117	118	119

SIGNALS

0	READY
11	F2_START
108	FN_END
119	DONE

